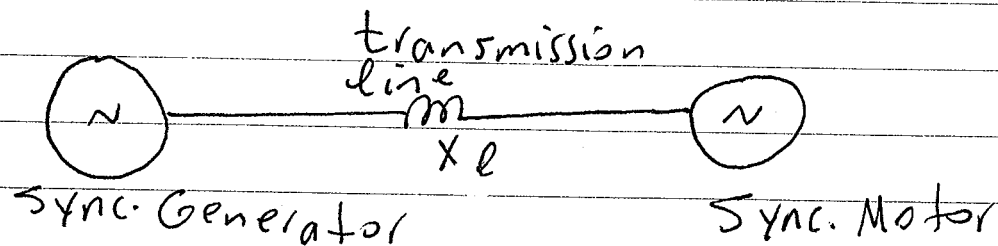


Prob 1: Consider the power system shown below.

$\frac{10}{20}$



The ratings of the components are:

Generator

100 MVA,

20 kV

P.u.

$X'_d = 0.25$

Motor

100 MVA

20 kV

$X'_d = 0.25$

Line

20 kV

$X_l = 0.2$  P.u.

Where the line impedance in p.u. is given assuming  $S_B = 100 \text{ MVA}$ ,  $V_B = 20 \text{ kV}$ . The motor is taking 100 MVA at 20 kV with power factor 1. Assume a 3-phase short circuit fault at the motor terminal.


Find the transient currents for both the generator and the motor.

Prob 2: In prob 1, assume the motor is not receiving any power. For the same fault find both subtransient and transient currents of the motor and the generator assuming  $X''_d = 0.1$  P.u. for both machines.

$\frac{10}{20}$

ECE 4620/5620 [Q2; SP 2013]; Key

Prob 1

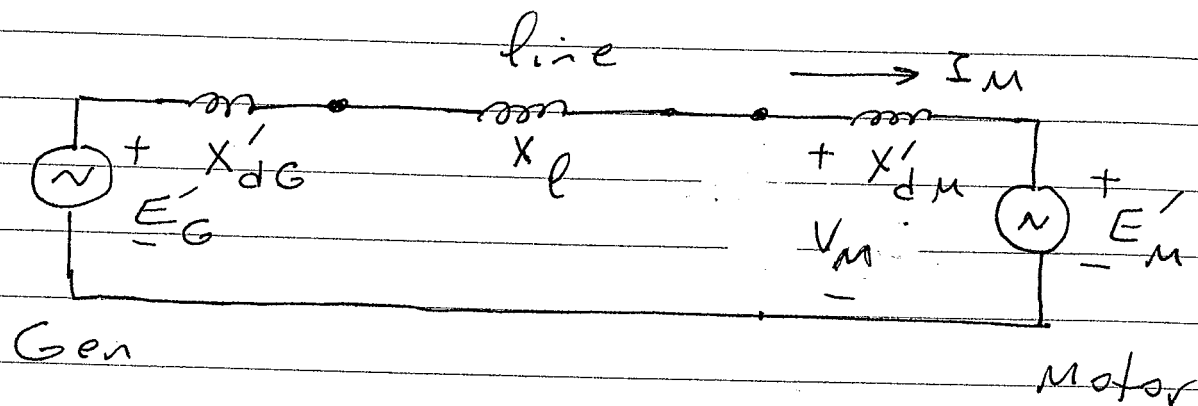

Given the base power and base voltage for all equipments are the same as their ratings and are equal, the p.u. - values for the reactances need not be recalculated.

Before Fault:

$$\begin{cases} S_M = 100 \text{ MVA}; \text{ Pf} = 1 \\ V_M = 20 \text{ kV} \end{cases}$$

or,

$$S_M = \frac{100 \text{ MVA}}{S_B} = \frac{100}{100} = 1 \text{ p.u.}$$

$$V_M = \frac{20 \text{ kV}}{V_B} = \frac{20 \text{ kV}}{20 \text{ kV}} = 1 \text{ p.u.}$$

$\Rightarrow$

$$I_M = \left( \frac{S_M}{V_M} \right) \angle -\cos^{-1}(\text{Pf})$$

$$= \frac{1}{1} \angle -\cos^{-1}(1) = 1 \angle 0 \text{ p.u.}$$

Now, using this prefault current we find  $E'_M$  and  $E'_G$  as follows:

$$E'_M = V_M - j X'_{dM} \cdot I_M$$

$$= 1 - j (0.25) (1) = 1 - j 0.25$$


$$= 1.03 \angle -14.04$$

$$E'_G = j (X'_{dG} + X_\ell) I_M + V_M$$

$$= j (0.25 + 0.2) (1) + 1$$

$$= 1 + j 0.45 = 1.1 \angle 24.23$$

During transient period of the fault:

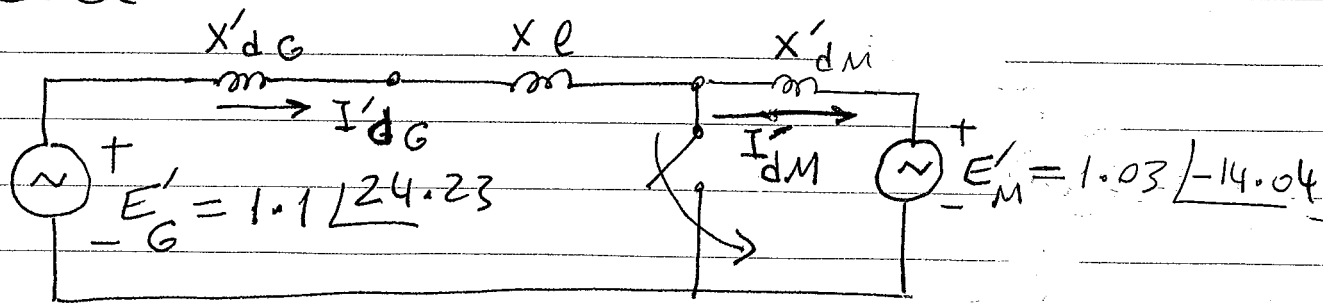

$$I'_{dG} = \frac{+E'_G}{j(X'_{dG} + X_\ell)} ; \text{ from the left loop}$$

$$= \frac{+1.1 \angle 24.23}{j(0.25 + 0.2)} = \frac{1.1 \angle 24.23}{0.45 \angle 90} = 2.44 \angle -65.79^\circ$$

$$I'_{dM} = \frac{-E'_M}{j X'_{dM}} ; \text{ from the right loop.}$$


Note the direction of the motor current has changed.

$$= \frac{-1.03 \angle -14.04}{j 0.25} = -4.12 \angle -114.04$$

Note motor current during the fault is a lot larger than the generator current since it is closer to fault
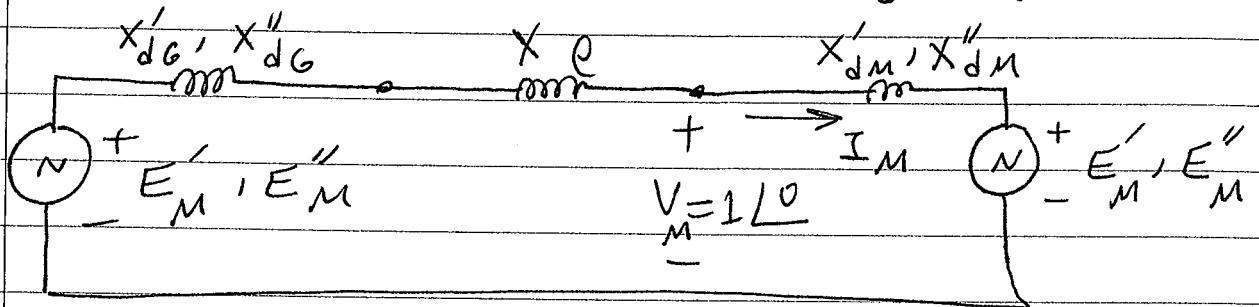
## Prob 2

Before fault: we have  $I_M = 0$  since the motor is not receiving any power.



Given  $V_M = 1\angle 0$  and  $I_M = 0$ , the voltage at all points must be the same as  $V_M$ ; or,


$$\rightarrow E'_M = V_M - j(X'_{dM})I_M^{\leftarrow=0} = V_M = 1\angle 0$$

$$\rightarrow E''_M = V_M - j(X''_{dM})I_M = \dots = 1\angle 0$$

$$\rightarrow E'_G = V_M + j(X_l + X'_{dG})I_M = \dots = 1\angle 0$$

$$\rightarrow E''_G = V_M + j(X_l + X''_{dG})I_M = \dots = 1\angle 0$$

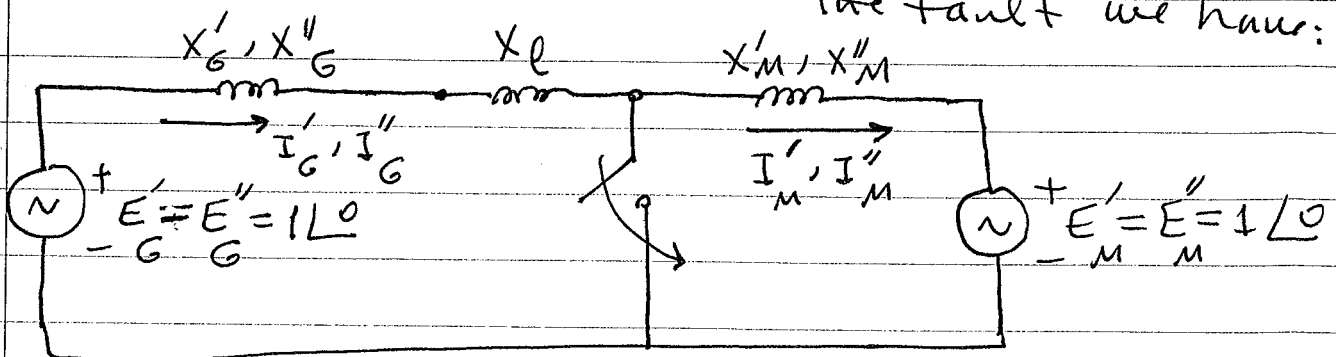During the transient and subtransient periods of the fault we have:



$$I'_G = \frac{E'_G}{j(X'_G + X_\ell)} = \frac{1 \angle 0}{j(0.25 + 0.2)}$$

$$= \frac{1 \angle 0}{j 0.45} = -j 2.22 \text{ p.u.}$$

$$I''_G = \frac{E''_G}{j(X''_G + X_\ell)} ; X''_G = X''_d = 0.1 \text{ was given}$$

$$= \frac{1 \angle 0}{j(0.1 + 0.2)}$$

$$= \frac{1 \angle 0}{j 0.3} = -j 3.33 \text{ p.u.}$$

$$I'_M = \frac{-E'_M}{jX'_M} = \frac{-1 \angle 0}{j 0.25} = j 4 \text{ p.u.}$$

$$I''_M = \frac{-E''_M}{jX''_M} ; X''_M = X''_d = 0.1 ; \text{ was given}$$

$$= \frac{-1 \angle 0}{j(0.1)}$$

$$= j 10 ; \text{ p.u.}$$