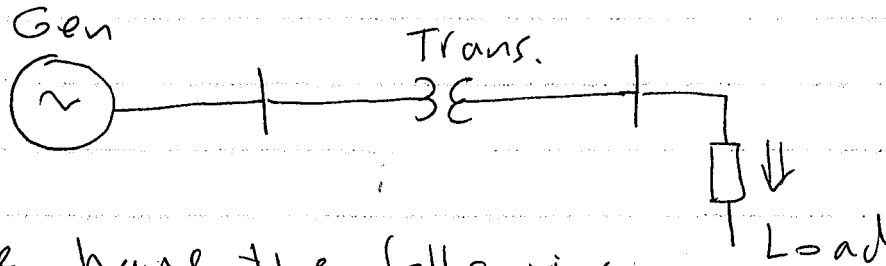


ECE 4620/5620 [Q2; SP 2013]; NO:
Name: _____

Prob 1: Consider the power system shown below:



We have the following parameters and ratings:

Gen: $X_d = 1.0$ p.u., $X'_d = 0.25$ p.u., $X''_d = 0.12$ p.u.
100-MVA, 13.8 kV, 60 Hz

Transformer: 13.8 kV / 220 kV, 100 MVA; $X_T = 0.2$ p.u.

Load: 220 kV, 100 MVA, $Pf = 0.8$ (lag)


The generator delivers 90 MVA at 220 kV to the load.

suddenly a 3-phase short circuit fault occurs at the generator terminal.
Find the generator current during:

a) subtransient (I''_d)

b) transient (I'_d)

c) long after transient period (I_d)

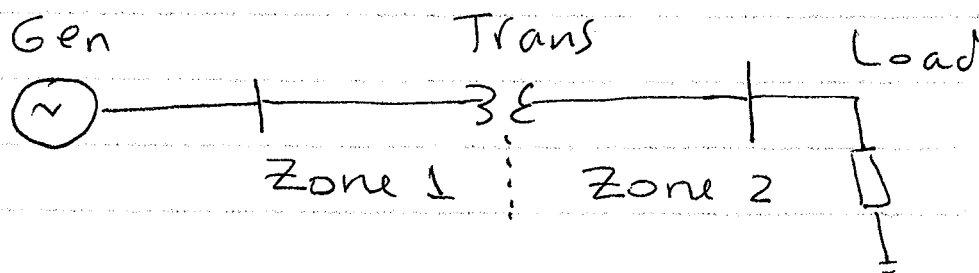Prob 1

Let's choose the system-wide base values as:

$$S_B = 100 \text{ MVA}, \quad V_{B1} = 13.8 \text{ kV}; \text{ for Zone 1}$$

With these base values the p.u. values of the reactances will not change.

Now, the base value in zone 2 is found as:

$$V_{B2} = \frac{220}{13.8} \quad V_{B1} = \frac{220}{13.8} \times 13.8 = 220 \text{ kV}$$

Now, the load is located in Zone 2, then:

$V_L \triangleq$ the load voltage


$$= 220 \text{ kV} = \frac{220 \text{ kV}}{V_{B2}} = \frac{220 \text{ kV}}{220} = 1 \text{ p.u.}$$

Choosing V_L as the reference voltage:

$$V_L = 1 \angle 0^\circ$$

$$S_L = 90 \text{ MVA} \angle \cos^{-1}(\text{pf}) = \frac{90}{100} \angle \cos^{-1}(0.8) \\ = 0.9 \angle 36.87^\circ; \text{ in p.u.}$$

• Prior to the fault we have:

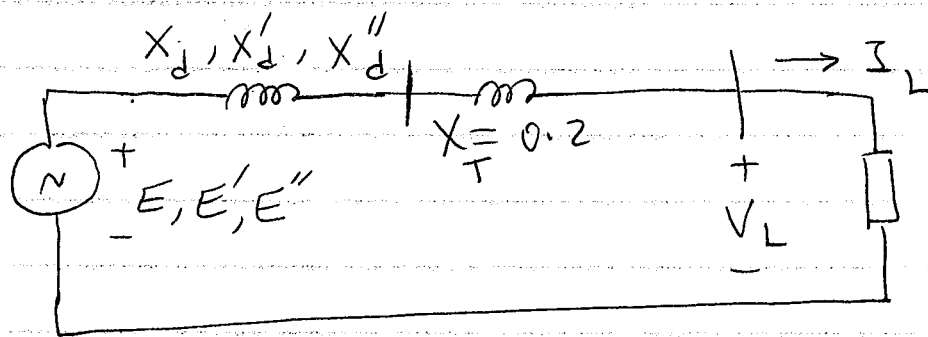

$$S_L = V_L I_L^* \Rightarrow I_L^* = \frac{S_L}{V_L}$$

$$\Rightarrow I_L = \frac{S_L^*}{V_L^*} = \frac{0.9 \angle -36.87}{1 \angle 0} = 0.9 \angle -36.87^\circ$$


Now,

$$\begin{aligned} \Rightarrow E &= (jX_d + jX_T) I_L + V_L \\ &= (j1 + j0.2)(0.9 \angle -36.87^\circ) + 1 \\ &= 1.08 \angle 53.13 + 1 = 0.65 + j0.86 + 1 \\ &= 1.65 + j0.86 = 1.86 \angle 27.53^\circ \end{aligned}$$

$$\begin{aligned} \Rightarrow E' &= (jX_d' + jX_T) I_L + V_L \\ &= (j0.25 + j0.2)(0.9 \angle -36.87^\circ) + 1 \\ &= 0.41 \angle 53.13 + 1 = 0.25 + j0.33 + 1 \\ &= 1.25 + j0.33 = 1.29 \angle 14.79^\circ \end{aligned}$$

$$\begin{aligned}
 \Rightarrow E'' &= (jX_d'' + jX_T) I_L + V_L \\
 &= (j0.12 + j0.2)(0.9 \angle -36.87^\circ) + 1 \\
 &= 0.29 \angle 53.13 + 1 = 0.17 + j0.23 + 1 \\
 &= 1.17 + j0.23 = 1.19 \angle 11.12^\circ
 \end{aligned}$$

During fault the circuit becomes:

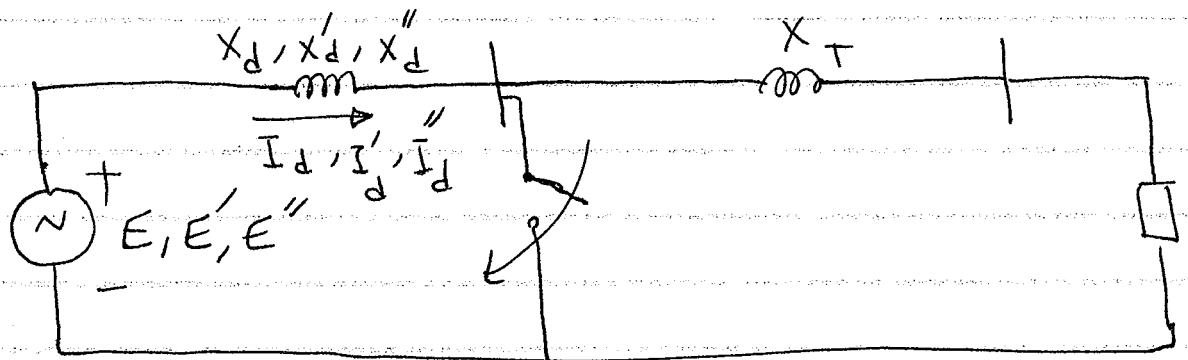

$$a) I_d'' = \frac{E''}{jX_d''} = \frac{1.19 \angle 11.12^\circ}{j0.12} = 9.92 \angle -78.88^\circ$$

$$b) I_d' = \frac{E'}{jX_d'} = \frac{1.29 \angle 14.79^\circ}{j0.25} = 5.16 \angle -75.21^\circ$$

$$c) I_d = \frac{E}{jX_d} = \frac{1.86 \angle 27.53^\circ}{j1} = 1.86 \angle -62.47^\circ$$