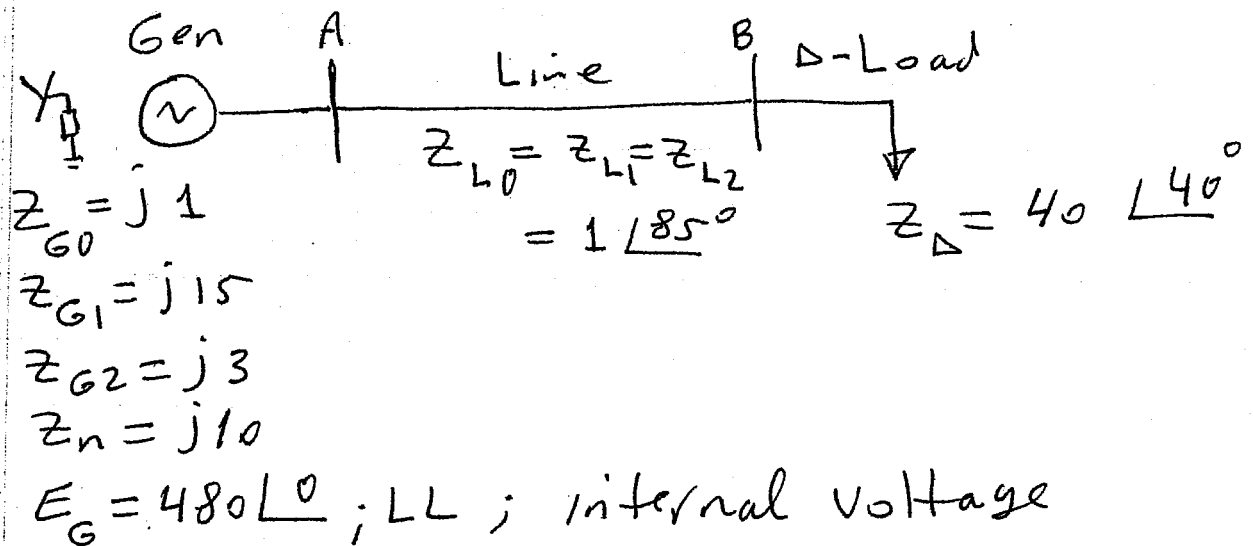


Example 2 <sup>examples</sup> [8-5, 6/Glover]

Consider the system shown by the Single-line-diag as:



- Draw the sequence networks and find the sequence currents and phase currents.
- Assume the generator is operating in unbalance condition with  $E_{G0}$ ,  $E_{G1}$ ,  $E_{G2}$ . The terminal voltage is given by:




$$\begin{bmatrix} V_{aA} \\ V_{bA} \\ V_{cA} \end{bmatrix} = \begin{bmatrix} 277 \angle 0^\circ \\ 260 \angle -120^\circ \\ 295 \angle 115^\circ \end{bmatrix}; \text{ unbalance voltage}$$

now, find the sequence currents through the sequence networks and the phase currents  $I_a, I_b, I_c$ .

- Find  $E_{G0}$ ,  $E_{G1}$ , and  $E_{G2}$ .

## Solution [Example 2]

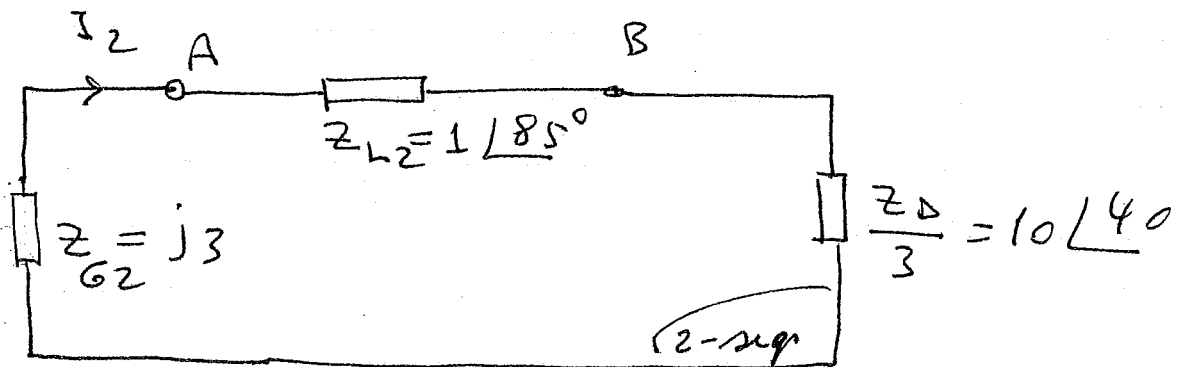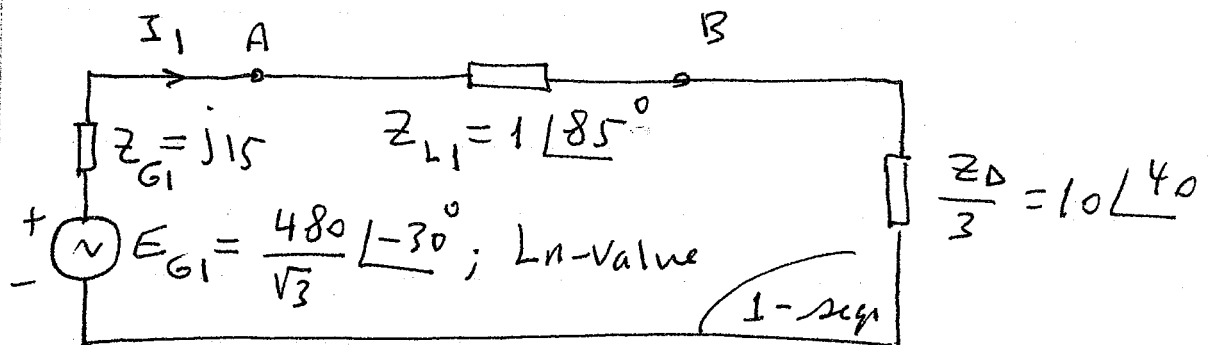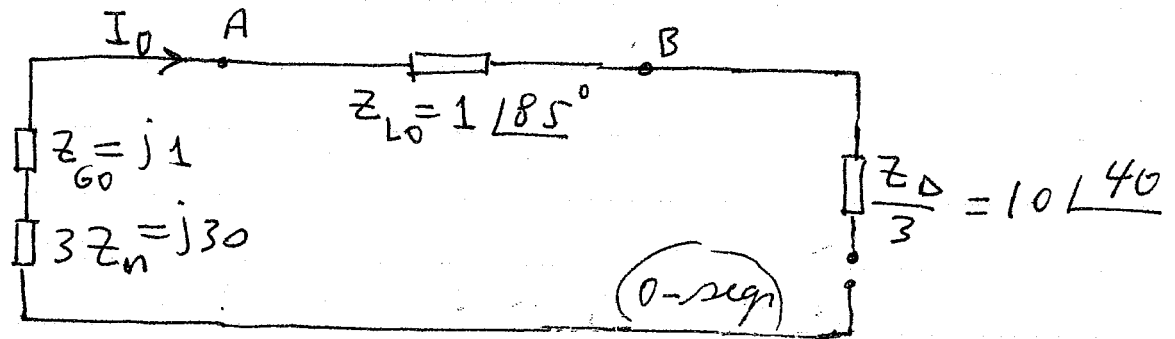- a) The sequence networks are obtained by connecting seq ckt's of all components together:



⇒

$$\left\{ \begin{array}{l} I_0 = 0 ; \text{ Since there is no source in that ckt and/or the ckt is open.} \\ I_1 = E_{G1} / [Z_{G1} + Z_{L1} + Z_D/3] = \dots = 25.83 \angle -73.78^\circ \\ I_2 = 0 ; \text{ Since there is no source in this ckt} \end{array} \right.$$

(over)

now,

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

$$= \dots = \begin{bmatrix} I_1 \\ a^2 I_1 \\ a I_1 \end{bmatrix} = \begin{bmatrix} 25.83 \angle -73.78 \\ 25.83 \angle -73.78 - 120 \\ 25.83 \angle -73.78 + 120 \end{bmatrix}$$

which gives a 3-phase balanced current (as expected)

b) In this case we are assuming for some reason the voltage at generator terminal is not balanced; the phase-values are given:

• Let's find the seq-values of the 3- $\phi$  voltage at terminal A:

$$\begin{bmatrix} V_{0A} \\ V_{1A} \\ V_{2A} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_{aA} \\ V_{bA} \\ V_{cA} \end{bmatrix}$$

$\Rightarrow$

$$\left\{ \begin{aligned} V_{0A} &= \frac{1}{3} (V_{aA} + V_{bA} + V_{cA}) = \dots = 15.91 \angle 62.11^\circ \\ V_{1A} &= \frac{1}{3} (V_{aA} + a V_{bA} + a^2 V_{cA}) = \dots = 277.1 \angle -1.7^\circ \\ V_{2A} &= \frac{1}{3} (V_{aA} + a^2 V_{bA} + a V_{cA}) = \dots = 9.22 \angle 216.59^\circ \end{aligned} \right.$$

(b) - [continued]

now, use these values in the seq-  
networks:

$$\Rightarrow I_0 = 0; \text{ since the ckt is open}$$

$$\Rightarrow I_1 = \frac{V_{1A}}{Z_{L1} + \frac{Z_{\Delta}}{3}} = \dots = 25.82 \angle -45.55^\circ$$

$$\Rightarrow I_2 = \frac{V_{2A}}{Z_{L2} + \frac{Z_{\Delta}}{3}} = \dots = 0.86 \angle 172.81^\circ$$

using the above sequence currents,  
we find the phase currents:





$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}; \begin{matrix} I_0, I_1, I_2 \\ \text{found above} \end{matrix}$$

$$\vdots \begin{bmatrix} 25.15 \angle -46.76^\circ \\ 25.71 \angle 196.34^\circ \\ 26.62 \angle 73.77^\circ \end{bmatrix}$$

c) The sequence network with  
unbalanced operation of the  
generator is as follows:

(over)

c) [continued]

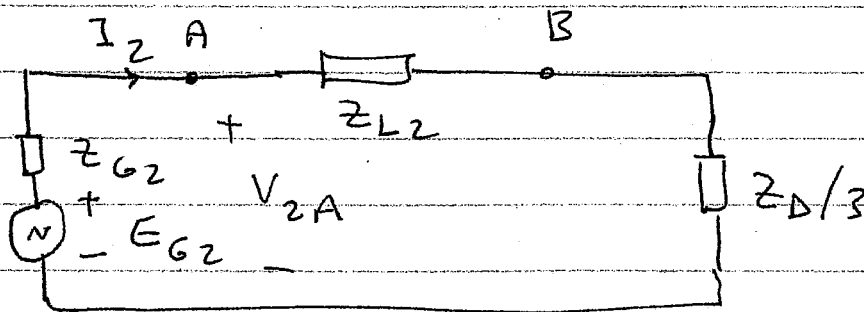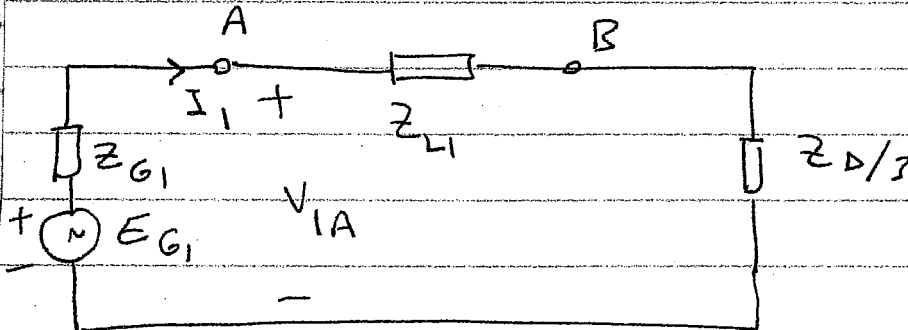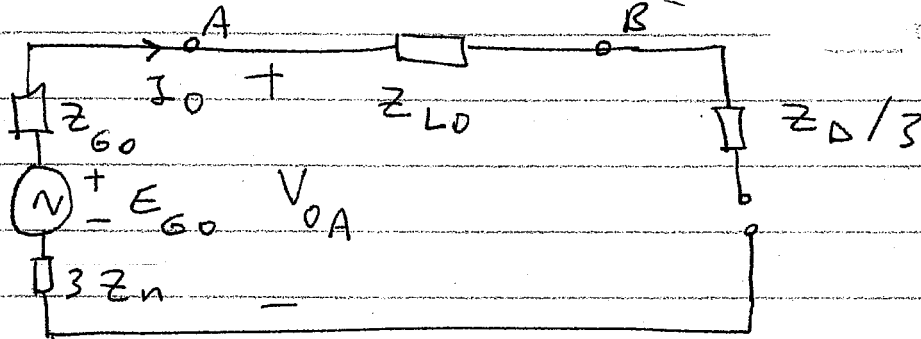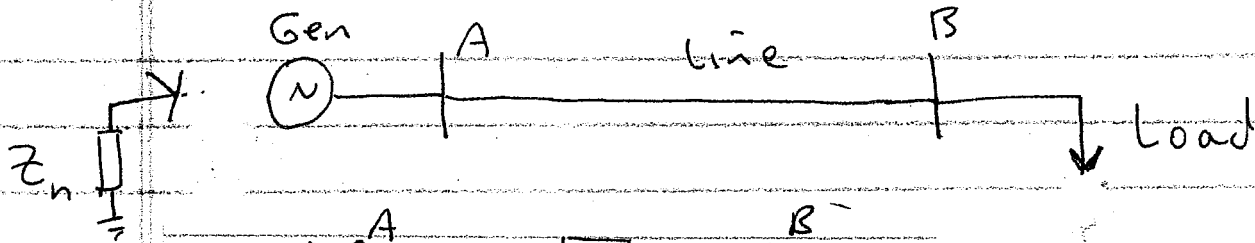

$$E_{G0} = Z_{G0} \cdot I_0 + V_{0A} = 0 + V_{A0} = 15 \cdot 91 \angle 62.11$$

$$E_{G1} = Z_{G1} I_1 + V_{1A} = \dots$$

just plug in numbers

$$E_{G2} = Z_{G2} I_2 + V_{2A} = \dots$$